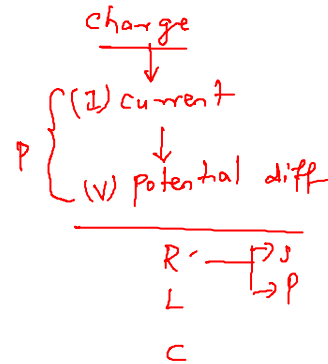


Unit - I

Introduction and Basic Concepts

Dr.Santhosh.T.K.




Progress Through Quality Education

1

Circuit Elements

- A circuit element usually has two terminals (sometimes three or more).
- The relationship between the voltage v across the terminals and the current i through the device defines the circuit element model.


Abstraction

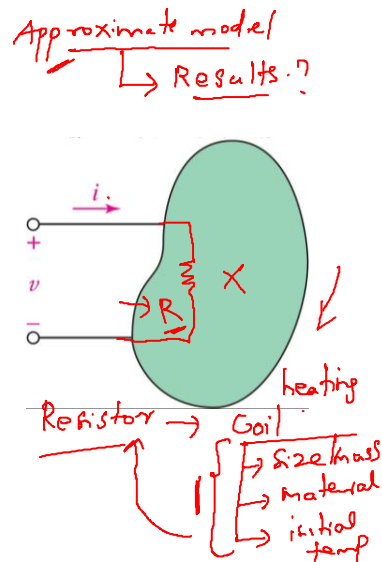

Progress Through Quality Education

Linear Elements and Circuits

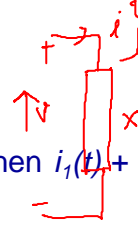
- a linear circuit element has a linear voltage-current relationship:
 - if $i(t)$ produces $v(t)$, then $Ki(t)$ produces $Kv(t)$
 - if $i_1(t)$ produces $v_1(t)$ and $i_2(t)$ produces $v_2(t)$, then $i_1(t) + i_2(t)$ produces $v_1(t) + v_2(t)$
- resistors, sources are linear elements¹
- a linear circuit is one with only linear elements



¹Dependent sources need linear control equations to be linear elements.


Voltage Sources

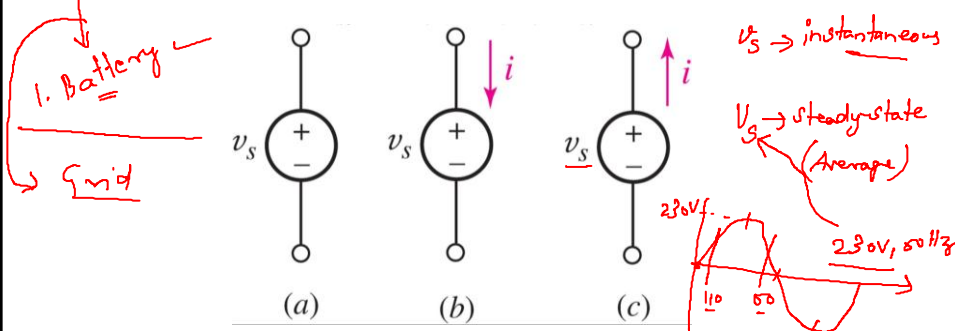- An ideal voltage source is a circuit element that will maintain the specified voltage v_s across its terminals. $\begin{cases} V \\ I \end{cases}$
- The current will be determined by other circuit elements.



Current Sources

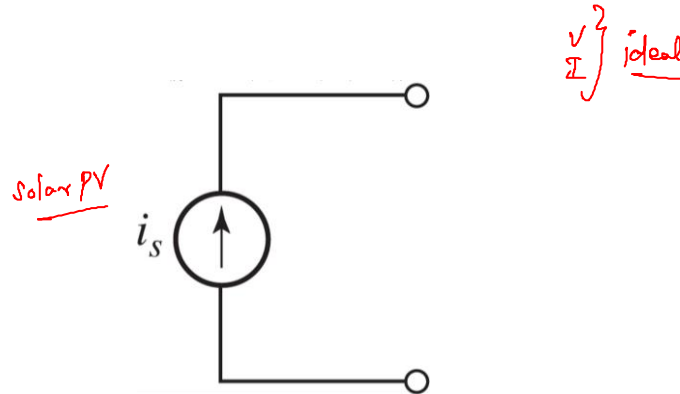
- An ideal current source is a circuit element that maintains the specified current flow i_s through its terminals.
- The voltage is determined by other circuit elements.



Progress Through Quality Education

Battery as Voltage Source

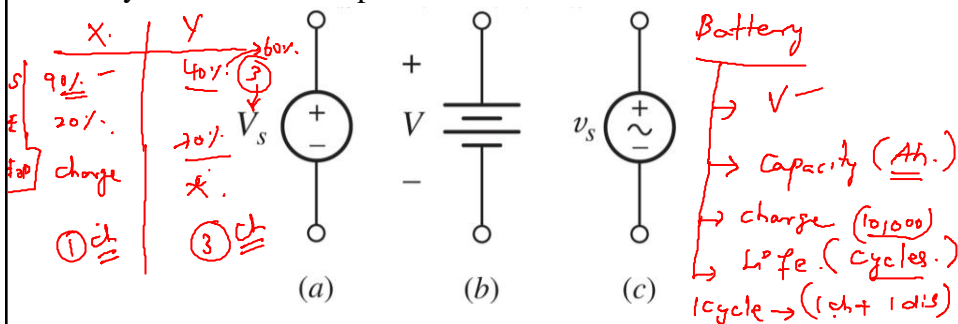
- A BM's voltage source is an idealization (no limit on current) and generalization (voltage can be time-varying) of a battery.
- A Battery supplies a constant "dc" voltage V but in practice a battery has a maximum power.



Progress Through Quality Education

Dependent Sources →

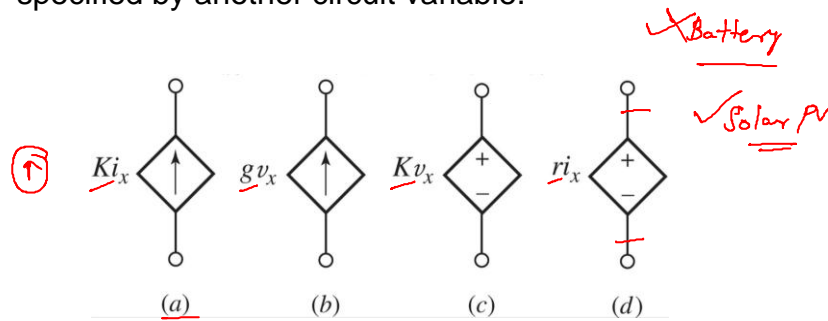
- Dependent current sources (a) and (b) maintain a *current* specified by another circuit variable.
- Dependent voltage sources (c) and (d) maintain a *voltage* specified by another circuit variable.



Progress Through Quality Education

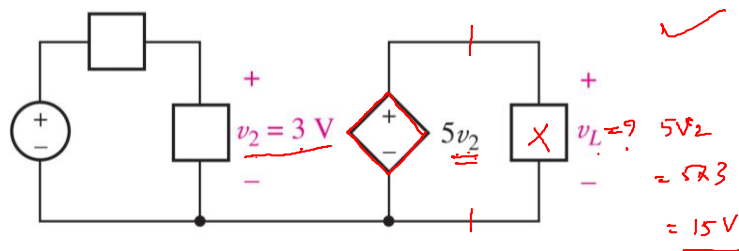Example: Dependent Sources

Find the voltage v_L in the circuit below.




Progress Through Quality Education

Ohm's Law: Resistance

- A (linear) resistor is an element for which

$$v=iR$$

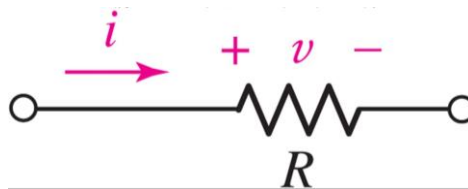- where the constant R is a resistance.
- The equation is known as "Ohm's Law."
- The unit of resistance is ohm (Ω).



Progress Through Quality Education

Resistors


- (a) typical resistors (b) power resistor
(c) a 10 T Ω resistor (d) circuit symbol




(a)



(b)

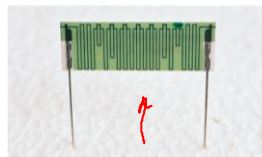

(c)

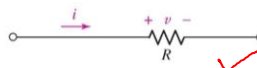


(d)

Progress Through Quality Education

The i-v Graph for a Resistor

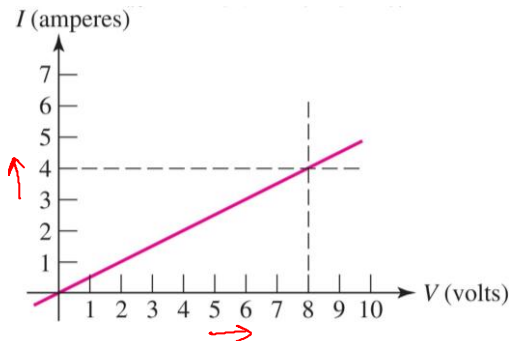For a resistor, the plot of current versus voltage is a straight line:



In this example, the slope is 4 A / 8 V or $0.5 \Omega^{-1}$.

This is the graph for a 2 ohm resistor.

Progress Through Quality Education

Power Absorption

Resistors absorb power: since $v=iR$

$$\checkmark p = \underline{vi} = \underline{v^2/R} = \underline{i^2 R}$$

Positive power means the device is absorbing energy.
Power is always positive for a resistor!



Progress Through Quality Education

Example: Resistor Power

A $560\ \Omega$ resistor is connected to a circuit which causes a current of 42.4 mA to flow through it. Calculate the voltage across the resistor and the power it is dissipating.

$$v = iR = (0.0424)(560) = 23.7\text{ V}$$

$$p = i^2 R = (0.0424)^2(560) = 1.007\text{ W}$$

$$v = iR \quad \text{--- (1)}$$

$$P = v \cdot i \quad \text{--- (2)}$$


$$R = 560\ \Omega$$

$$i = 42.4\text{ mA}$$

Power


$$P = v \cdot i$$

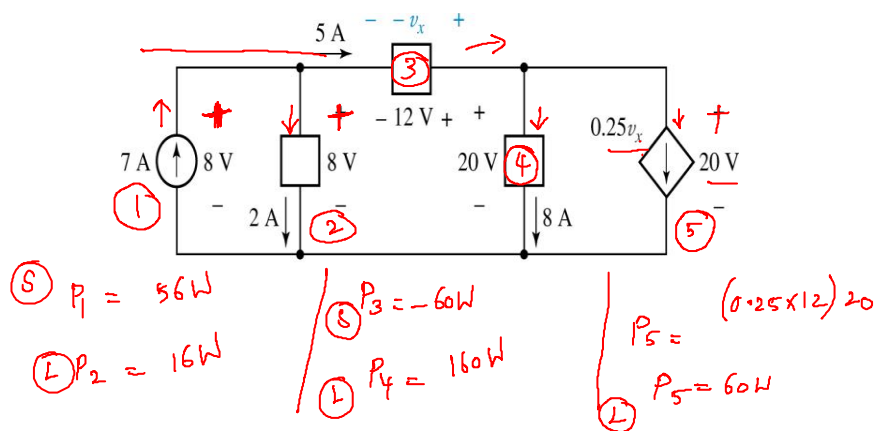Find the power absorbed by each element in the circuit below.



Wire Gauge and Resistivity

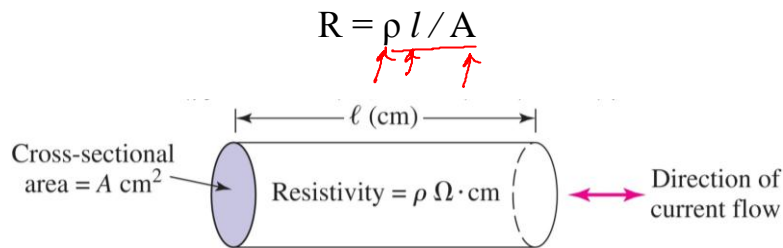The resistance of a wire is determined by the resistivity of the conductor as well as the geometry:



[In most cases, the resistance of wires can be assumed to be 0 ohms.]

Conductance


- We sometimes prefer to work with *the reciprocal of resistance* ($1/R$), which is called conductance (symbol G , unit siemens (S)).
- A resistor R has conductance $\underline{G=1/R}$.
- The i - v equation (i.e. Ohm's law) can be written as

$$i = Gv$$



SASTRA
DEEMED TO BE UNIVERSITY
SASTRA DEEMED TO BE UNIVERSITY
SASTRA DEEMED TO BE UNIVERSITY

Variable Resistor: Rotary Potentiometers

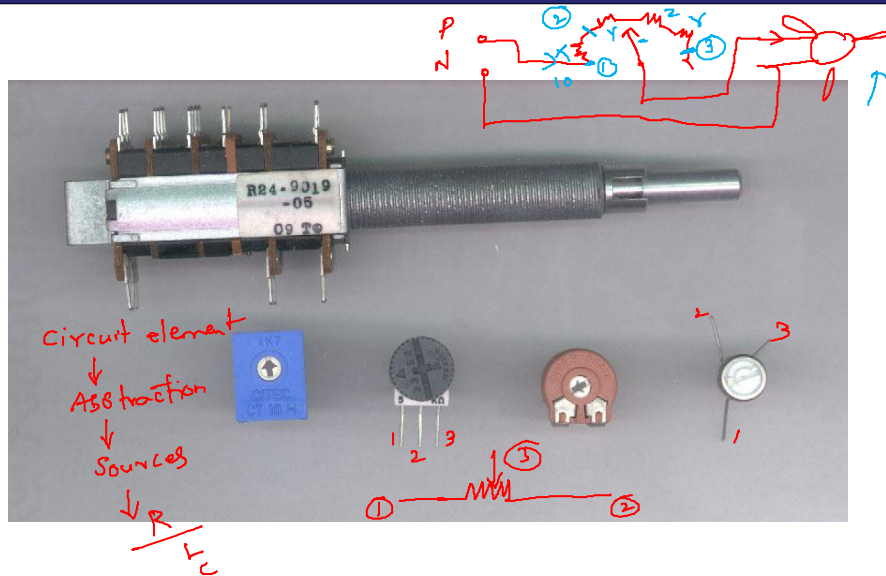

Progress Through Quality Education

17