

## Unit - II

### 2.3 Mesh Analysis

Dr.Santhosh.T.K.

1

Li-ion

Sodium ion battery

L → cylindrical height  
 NCR 26 650-2300 → dia capacity  
 ↓ → copper  
 26 650 → 1500mAh.  
 2300mAh.

'c' rate

1C → CC

3C → 7.36W

0-55

-20 to +55

Tool chest

## Syllabus

### UNIT – II


14 Periods

**DC Circuit Analysis:** Voltage source and current sources, ideal and practical, Kirchhoff's laws and applications to network solutions using mesh analysis, - Simplifications of networks using series- parallel, Star/Delta transformation, DC circuits-Current-voltage relations of electric network by mathematical equations to analyse the network (Superposition theorem, Thevenin's theorem, Maximum Power Transfer theorem), Transient analysis of R-L, R-C and R-L-C Circuits.

**AC Steady-state Analysis:** AC waveform definitions - Form factor - Peak factor - study of R-L - R-C -RLC series circuit - R-L-C parallel circuit - phasor representation in polar and rectangular form - concept of impedance - admittance - active - reactive - apparent and complex power - power factor, Resonance in R-L-C circuits - 3 phase balanced AC Circuits

Progress Through Quality Education

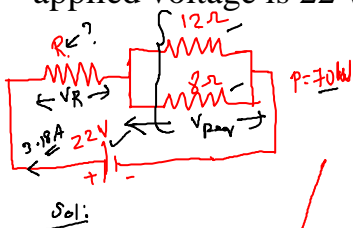- A resistance R is connected in series with a parallel circuit comprising two resistor  $12\ \Omega$  and  $8\ \Omega$  respectively. The total power dissipated in the circuit is  $70\text{ W}$ . When the applied voltage is  $22\text{ volts}$ . Calculate the value of R.



Sol:

$$P = V \cdot I$$

$$I = \frac{P}{V} = \frac{70}{22} = 3.18\text{ A}$$

$$R_{\text{eq}} = \frac{12 \times 8}{12 + 8} = 4.8\ \Omega$$

Voltage across  $R_{\text{eq}}$

$$= 3.18 \times 4.8$$

$$= 15.26\text{ V}$$

$$22 - V_R - 15.26 = 0$$

$$V_R = 6.73\text{ V}$$

$$R = \frac{V}{I} = \frac{6.73}{3.18} = 2.12\ \Omega$$


$$R = 2.12\ \Omega$$

Progress Through Quality Education


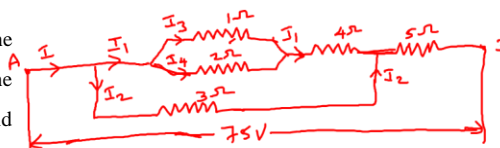
## Practice Problem

- Determine the effective resistance of the series-parallel combination shown in the figure. Also, find the current, voltage and power dissipated in each of the resistor in the given circuit.



$$R_{eq} = 15.7/23 \Omega \quad I_3 \approx 2.86 A$$

$$I = 10.98 A \quad I_4 \approx 1.43 A$$

$$I_1 \approx 4.3 A$$


$$I_2 \approx 6.78 A$$



## Practice Problem

Find the load current in the given circuit (Use KVL).

KVL → Loops → 3 loops

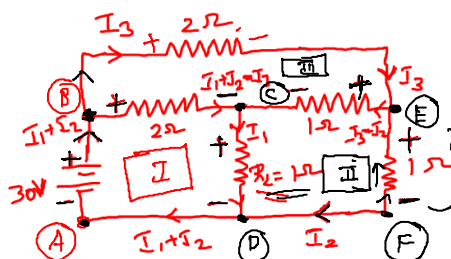

Loop I : (A B C D A)

$$30 - (I_1 + I_2 - I_3)2 - I_1 = 0$$

Loop II (E C D F E)

$$-(I_3 - I_2)1 - I_1 + I_2 = 0$$

Loop III (B E C B)

$$-2I_3 - 1(I_3 - I_2) + 2(I_1 + I_2 - I_3) = 0$$

✓ Assume branch voltage & current  
Loop → ABCDA }  
E C D F E }  
B E C B }

AB C E F D A  
A B E F D A

$$I_1 = 8.49$$

$$I_2 = 10 A$$

$$I_3 = 10 A$$

load current  
 $I_L = 10 A$

## Mesh/Loop Analysis


- Loop analysis is developed by applying KVL around loops in the circuit
- Loop (mesh) analysis results in a system of linear equations which must be solved for unknown currents

Loop  $\rightarrow$  any closed path.

Mesh  $\rightarrow$  a loop that can't be subdivided
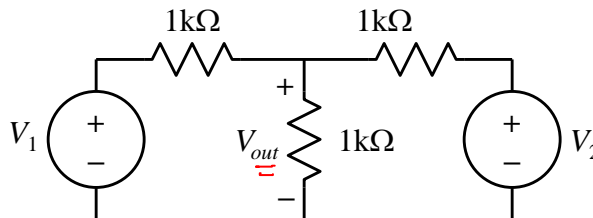
## Summing Circuit


- The output voltage  $V$  of this circuit is proportional to the sum of the two input voltages  $V_1$  and  $V_2$



## Steps of Mesh Analysis

1. Identify mesh (loops).
2. Assign a current to each mesh.
3. Apply KVL around each loop to get an equation in terms of the loop currents.
4. Solve the resulting system of linear equations for the mesh/loop currents.


## 1. Identifying the Meshes

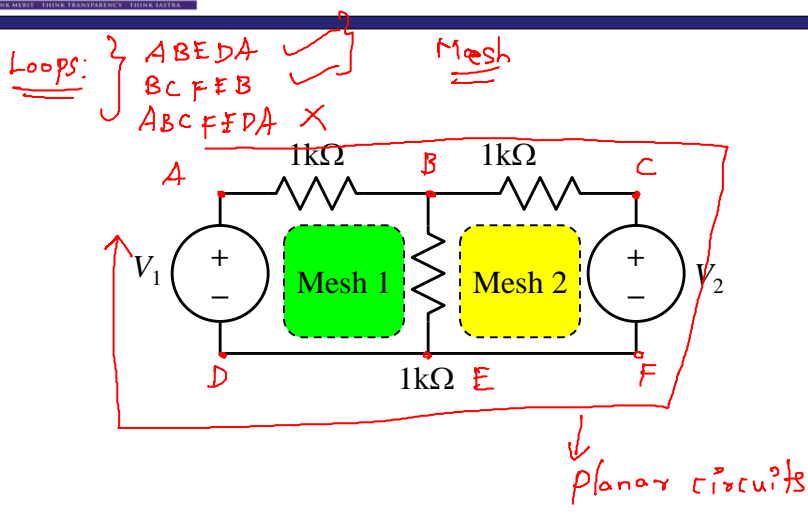

## Steps of Mesh Analysis

1. Identify mesh (loops).
2. **Assign a current to each mesh.** ②
3. Apply KVL around each loop to get an equation in terms of the loop currents.
4. Solve the resulting system of linear equations for the mesh/loop currents.


## 2. Assigning Mesh Currents

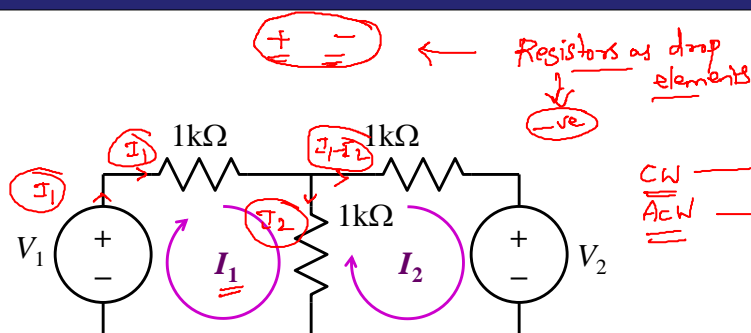


## Steps of Mesh Analysis

1. Identify mesh (loops).
2. Assign a current to each mesh.
- 3. Apply KVL around each loop to get an equation in terms of the loop currents.**
4. Solve the resulting system of linear equations for the mesh/loop currents.

## Voltages from Mesh Currents

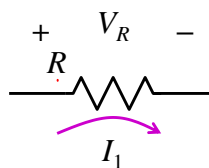

$$V_R = \underline{I_1} R$$

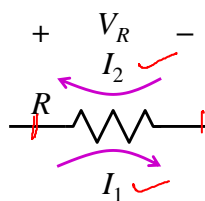


$$V_R = \underline{(I_1 - I_2)} R \rightarrow \text{Mesh 1}$$


$$V_R = \underline{(I_2 - I_1)} R \leftarrow \text{Mesh 2}$$



### 3. KVL Around Mesh 1

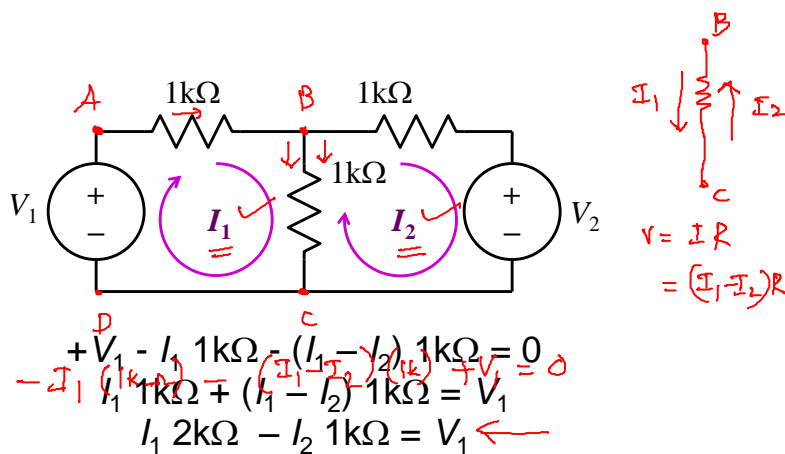

### 3. KVL Around Mesh 2

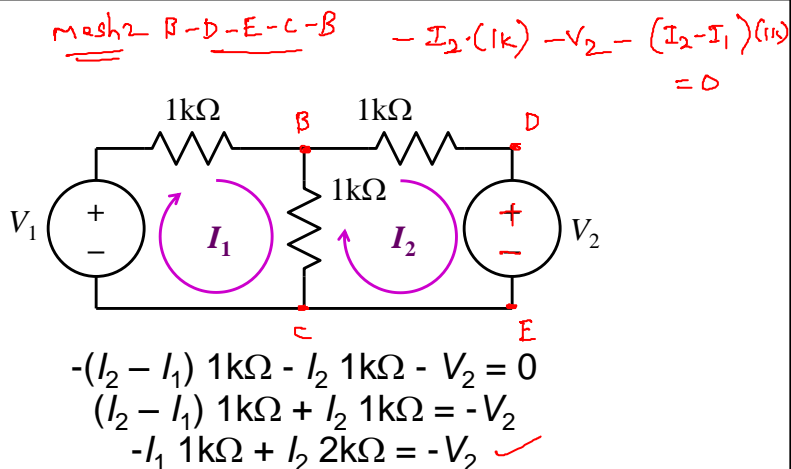



## Steps of Mesh Analysis

1. Identify mesh (loops).
2. Assign a current to each mesh.
3. Apply KVL around each loop to get an equation in terms of the loop currents.
- 4. Solve the resulting system of linear equations for the mesh/loop currents.**

## Matrix Notation

- The two equations can be combined into a single matrix/vector equation

$$I_1 2k\Omega - I_2 1k\Omega = V_1$$


$$-I_1 1k\Omega + I_2 2k\Omega = -V_2$$

$$\begin{bmatrix} 1k\Omega + 1k\Omega & \textcircled{-1k\Omega} \\ \textcircled{-1k\Omega} & 1k\Omega + 1k\Omega \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \end{bmatrix}$$

$\underline{\underline{R}} \quad I = V$



## Inspection Method

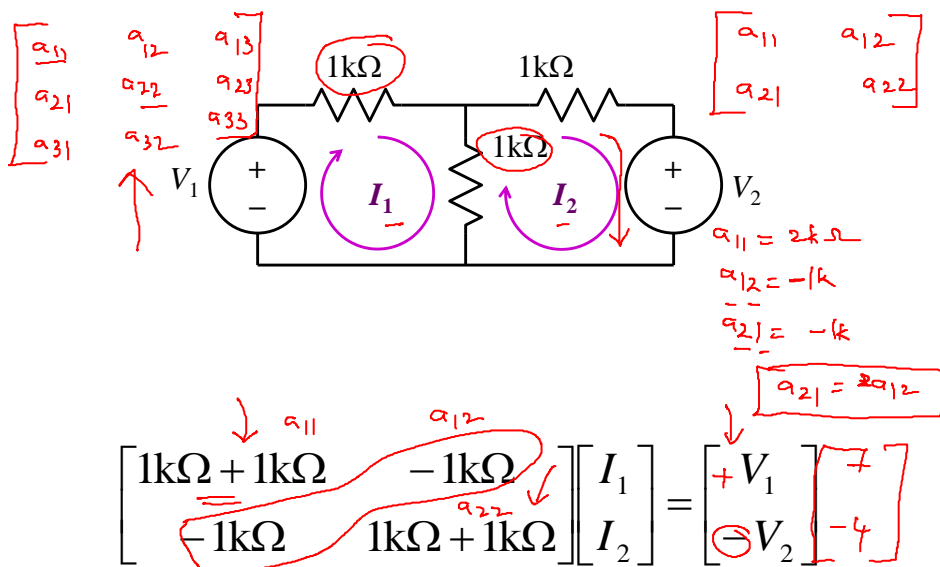

## 4. Solving the Equations

Let:  $V_1 = 7V$  and  $V_2 = 4V$

Results:

$$I_1 = 3.33 \text{ mA}$$

$$I_2 = -0.33 \text{ mA}$$

Finally

$$V_{out} = (I_1 - I_2) 1k\Omega = 3.66V$$

Handwritten calculations:

$$3.334 \text{ mA}$$

$$0.334 \text{ mA}$$

$$I_1 = 3.334 \text{ mA}$$

$$I_2 = -0.334 \text{ mA}$$


$$I_1 - I_2 = 3.668 \text{ mA}$$

$$3.668 \text{ mA} \times 1k\Omega = 3.668V$$


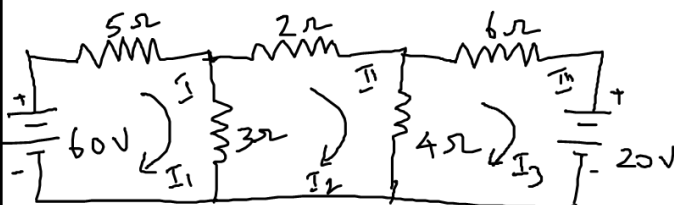
## Practice Problem

Determine the power dissipation in the  $4\Omega$  resistor of the given network.



## Summary

KVL, KCL

→ branch  $V/I$

→  $+- \rightarrow$  KVL  $\rightarrow$  Equation  $\rightarrow$  Unknowns.

