

Unit - I


1.8 Capacitors

Wireless power transmission

→ short distance → long distance

Dr.Santhosh.T.K.

Wireless Power Transmission

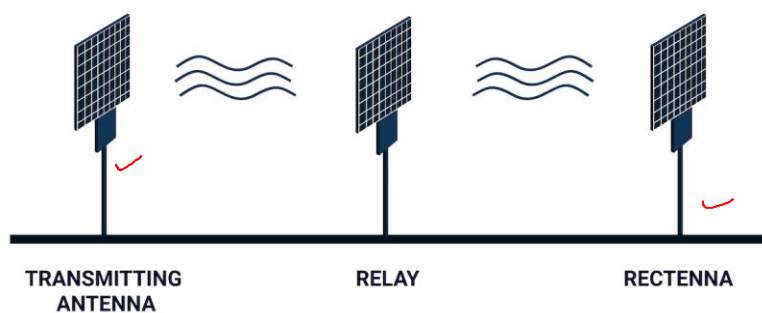

← Power →
<https://emrod.energy/wireless-power/>

Syllabus

UNIT – I

10 Periods


Introduction and Basic Concepts: Concept of Potential difference, voltage, current - Fundamental linear passive and active elements to their functional current-voltage relation - Terminology and symbols in order to describe electric networks - Concept of work, power, energy and conversion of energy- Principle of batteries and application.

Principles of Electrostatics: Electrostatic field - electric field intensity - electric field strength - absolute permittivity - relative permittivity - capacitor composite – dielectric capacitors - capacitors in series & parallel - energy stored in capacitors - charging and discharging of capacitors.

Capacitors: the basics

What is a capacitor?

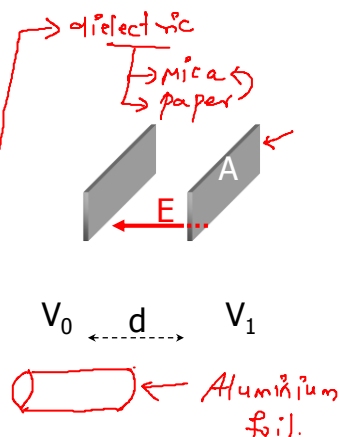- device for **storing charge**
- simplest example: two parallel conducting plates separated by air



assortment of capacitors



SASTRA
DEEMED TO BE UNIVERSITY
THINK WISE! THINK TRANSPARENTLY! THINK SASTRA!

Capacitance

How much charge can a capacitor store?

Better question: How much charge can a capacitor store per voltage?

Capacitance: $C = \frac{Q}{V}$

V is really $|\Delta V|$, the potential difference across the capacitor

capacitance C is a **device property**, it is always positive

unit of C: farad (F) ←

1 F is a large unit, most capacitors have values of C ranging from picofarads to microfarads (pF to μF). ←

micro $\Rightarrow 10^{-6}$, nano $\Rightarrow 10^{-9}$, pico $\Rightarrow 10^{-12}$ (Know for exam!)

Progress Through Quality Education




SASTRA
DEEMED TO BE UNIVERSITY
THINK WISE! THINK TRANSPARENTLY! THINK SASTRA!

Capacitance of parallel plate capacitor

electric field between two parallel charged plates:

$$E = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$$

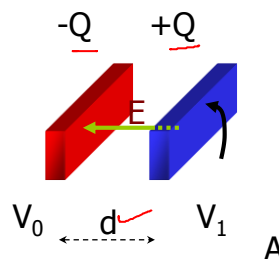Q is magnitude of charge on either plate.



potential difference:

$$\Delta V = V_1 - V_0 = -\int_0^d \vec{E} \cdot d\vec{\ell} = E \int_0^d dx = Ed$$

capacitance:

$$C = \frac{Q}{\Delta V} = \frac{Q}{Ed} = \frac{Q}{\left(\frac{Q}{\epsilon_0 A}\right)d} = \frac{\epsilon_0 A}{d}$$

Progress Through Quality Education

Example: calculate the capacitance of a capacitor whose plates are 20 cm x 3 cm and are separated by a 1.0 mm air gap.


$$C = \frac{\epsilon_0 A}{d}$$

$$C = \frac{(8.85 \times 10^{-12})(0.2 \times 0.03)}{0.001} \text{ F}$$

$$C = 53 \times 10^{-12} \text{ F}$$

$$C = 53 \text{ pF} \quad \checkmark$$

$C =$

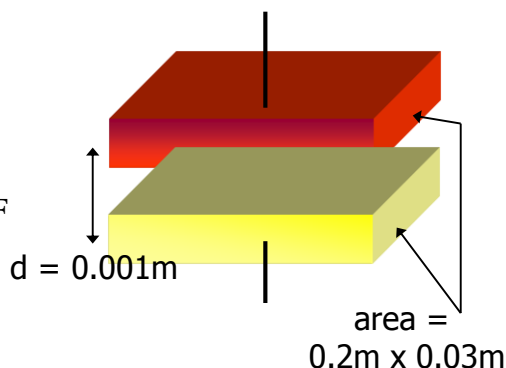

Progress Through Quality Education


Example: what is the charge on each plate if the capacitor is connected to a 12 volt* battery?

$$Q = CV$$

$$Q = (53 \times 10^{-12})(12) \text{ C}$$

$$Q = 6.4 \times 10^{-10} \text{ C} \quad \checkmark$$

$$Q = 637.2 \text{ pC}$$

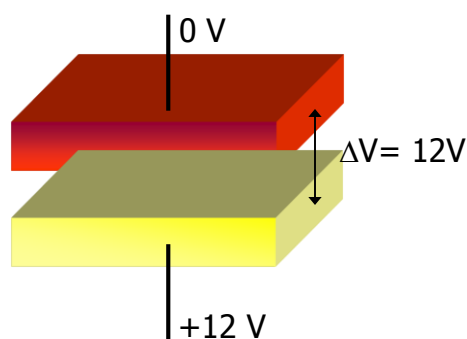

*Remember, it's the potential difference that matters.

Progress Through Quality Education




Example: what is the electric field between the plates?

$$E = \frac{\Delta V}{d}$$

$$E = \frac{12V}{0.001 \text{ m}}$$
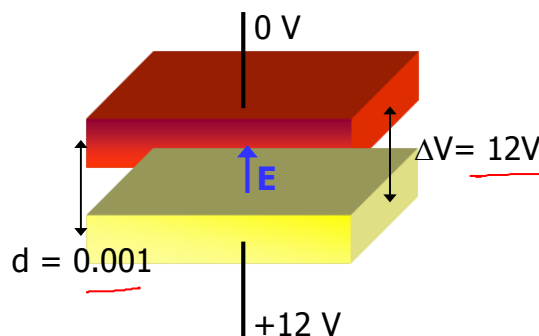
$$\vec{E} = 12000 \frac{\text{V}}{\text{m}}, \text{ "up."}$$



$$E = 12,000 \text{ V/m}$$

Progress Through Quality Education




Capacitors in Series and Parallel

	Parallel	Series
equivalent capacitance	$C_{eq} = \sum_i C_i$	$\frac{1}{C_{eq}} = \sum_i \frac{1}{C_i}$
charge	Q's add	V's add
voltage	same V	same Q →

Progress Through Quality Education


10

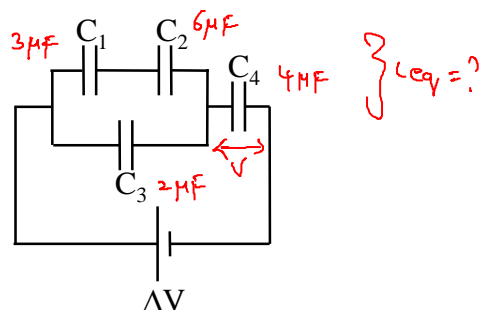Example: for the capacitor circuit shown, $C_1 = 3\mu\text{F}$, $C_2 = 6\mu\text{F}$, $C_3 = 2\mu\text{F}$, and $C_4 = 4\mu\text{F}$. (a) Find the equivalent capacitance. (b) if $\Delta V = 12\text{ V}$, find the potential difference across C_4 .



Progress Through Quality Education

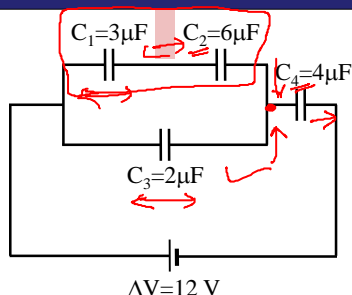(a) Find C_{eq} . (b) if $\Delta V = 12\text{ V}$, find V_4 .



C_1 and C_3 are not in parallel. Make sure you understand why!

C_2 and C_4 are not in series. Make sure you understand why!

C_1 & $C_2 \rightarrow$

C_1 and C_2 are in series. Make sure you use the correct equation!


C_1 & $C_3 \rightarrow$

$$\frac{1}{C_{12}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{3} + \frac{1}{6} = \frac{2}{6} + \frac{1}{6} = \frac{3}{6} = \frac{1}{2}$$

Don't forget to invert: $C_{12} = 2\mu\text{F}$.

Progress Through Quality Education

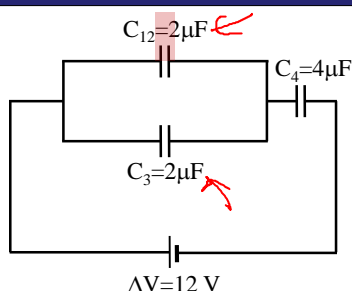(a) Find C_{eq} . (b) if $\Delta V = 12\text{ V}$, find V_4 .




C_{12} and C_4 are not in series. Make sure you understand why!

C_{12} and C_3 are in parallel. Make sure you use the correct equation!

$$C_{123} = C_{12} + C_3 = 2 + 2 = \underline{\underline{4\mu\text{F}}}$$

Progress Through Quality Education

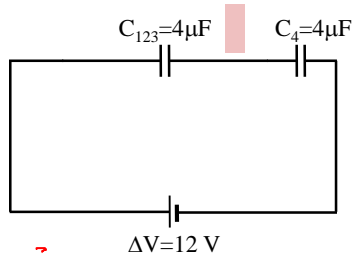(a) Find C_{eq} . (b) if $\Delta V = 12\text{ V}$, find V_4 .



$\checkmark R \rightarrow \Omega$ / $\checkmark C \rightarrow \text{RLC meter}$
 $\rightarrow \text{Measure} \rightarrow \text{Multimeter}$

C_{123} and C_4 are in series. Make sure you understand why! Combined, they make give C_{eq} .

$\checkmark C \rightarrow \text{RLC meter}$ $V_L = L \cdot \frac{dI}{dt}$

Batteries

$12\text{ V} / > 6\text{ V} \checkmark$

Make sure you use the correct equation!

$$\frac{1}{C_{eq}} = \frac{1}{C_{123}} + \frac{1}{C_{24}} = \frac{1}{4} + \frac{1}{4} = \frac{2}{4} = \frac{1}{2}$$


$< 6\text{ V} \times$

Don't forget to invert: $C_{eq} = \underline{\underline{2\mu\text{F}}}$

$\rightarrow \text{Working?}$
 $V_C = C \cdot \frac{dV}{dt}$

Progress Through Quality Education

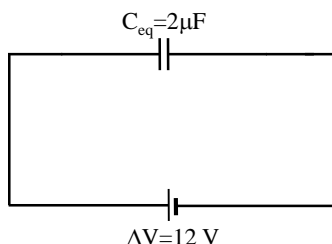(a) Find C_{eq} . (b) if $\Delta V = 12 \text{ V}$, find V_4 .




$$C_{eq} = 2 \mu\text{F}$$

If you see a capacitor circuit on the test, read the problem first. Don't go rushing off to calculate C_{eq} . Sometimes you are asked to do other things.

Truth in advertising: there's a high probability you will need to calculate C_{eq} at some point in the problem.

Progress Through Quality Education

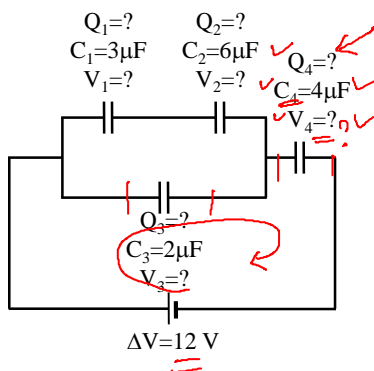(a) Find C_{eq} . (b) if $\Delta V = 12 \text{ V}$, find V_4 .



Hint: each capacitor has associated with it a Q , C , and V . If you don't know what to do next, near each capacitor, write down $Q =$, $C =$, and $V =$. Next to the $=$ sign record the known value or a "?" if you don't know the value. As soon as you know any two of Q , C , and V , you can determine the third. This technique often provides visual clues about what to do next.

$$C = \frac{Q}{V} \Rightarrow Q_4 = C_4 V_4$$


We know C_4 and want to find V_4 . If we know Q_4 we can calculate V_4 . Maybe that is a good way to proceed.

Progress Through Quality Education



SASTRA
DEEMED TO BE UNIVERSITY
THINK WISELY · THINK TRANSPARENTLY · THINK SASTRA

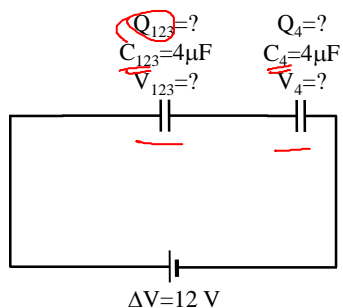(a) Find C_{eq} . (b) if $\Delta V = 12\text{ V}$, find V_4 .



C_4 is in series with C_{123} and together they form C_{eq} .

Therefore $Q_4 = Q_{123} = Q_{eq}$.

$$Q_{eq} = C_{eq} \Delta V = (2)(12) = 24 \mu\text{C} = Q_4$$

$$C = \frac{Q}{V} \Rightarrow V = \frac{Q}{C} \Rightarrow V_4 = \frac{Q_4}{C_4} = \frac{24}{4} = 6\text{V}$$

Progress Through Quality Education



SASTRA
DEEMED TO BE UNIVERSITY
THINK WISELY · THINK TRANSPARENTLY · THINK SASTRA

Capacitance of Concentric Spheres


If you have to calculate the capacitance of a concentric spherical capacitor of charge Q ...

In between the spheres (Gauss' Law)

$$E = \frac{Q}{4\pi\epsilon_0 r^2}$$

$$|\Delta V| = \frac{Q}{4\pi\epsilon_0} \int_a^b \frac{dr}{r^2} = \frac{Q}{4\pi\epsilon_0} \left[\frac{1}{a} - \frac{1}{b} \right]$$

$$C = \frac{Q}{|\Delta V|} = \frac{4\pi\epsilon_0}{\left[\frac{1}{a} - \frac{1}{b} \right]}$$

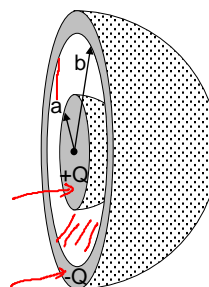

You need to do this derivation *if* you have a problem on spherical capacitors!

Progress Through Quality Education



Energy Stored in Electrostatic Field of Capacitance

- The electrostatic field of the charge stored in the dielectric has electric energy supplied by the voltage source that charges C .
- Energy = $\mathcal{E} = \frac{1}{2} CV^2$ (joules) ✓
 - ✓ C = capacitance (farads) ✓
 - ✓ V = voltage across the capacitor ✓
 - ✓ \mathcal{E} = electric energy (joules)
- Stored energy is the reason why a charged capacitor can produce electric shock even when it is not connected into a circuit.

Progress Through Quality Education



Problem

- A parallel plate capacitor with a plate of 0.25 m^2 and a plate separation of 6.00 mm is connected with 12 V source. Find:
 - (a) Charge on the capacitor ✓
 - (b) Energy stored in the capacitor ✓
 - (c) Potential difference across the capacitor is reduce to half, explain what will happen to charge on the capacitor and its stored energy ✓

Progress Through Quality Education

20

Solution

$$\begin{aligned}
 \text{(a)} \quad C &= \frac{\epsilon_0 A}{d} \\
 &= \frac{(8.854 \times 10^{-12})(0.25 \text{ m}^2)}{0.006 \text{ m}} \\
 &= 36.9 \times 10^{-9} \text{ F} \quad \checkmark
 \end{aligned}$$

$$\begin{aligned}
 \text{(b)} \quad U_c &= \frac{1}{2} CV^2 \\
 &= \frac{1}{2} (36.9 \times 10^{-9} \text{ F})(12 \text{ V})^2 \\
 &= 2.66 \times 10^{-6} \text{ J}
 \end{aligned}$$



$$E = \frac{1}{2} CV^2 = ?$$

$$\begin{aligned}
 \text{(c)} \quad &\text{Since } Q = CV, \text{ it half.} \\
 &\text{Since } U_C = \frac{1}{2} CV^2, \text{ it double.} \quad \frac{2}{4}
 \end{aligned}$$

Progress Through Quality Education

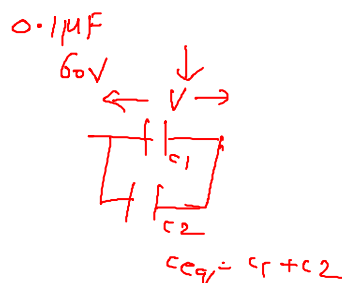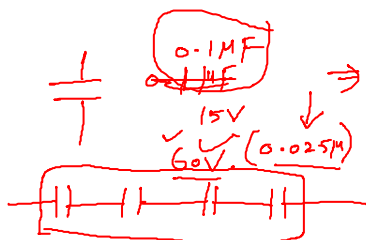Problem


- Given some capacitors of 0.1 μF capable of withstanding 15V. Calculate the number of capacitors needed if it is desired to obtain a capacitance of 0.1 μF for use in a circuit involving 60 V.



Progress Through Quality Education

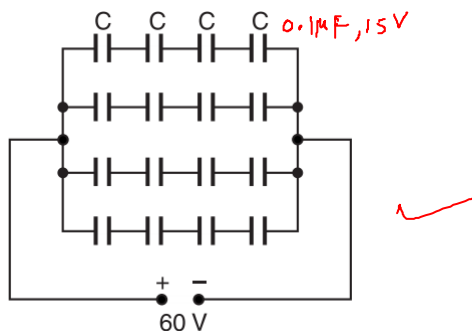Problem

- Given some capacitors of $0.1 \mu\text{F}$ capable of withstanding 15V . Calculate the number of capacitors needed if it is desired to obtain a capacitance of $0.1 \mu\text{F}$ for use in a circuit involving 60V .



Progress Through Quality Education

Summary

Capacitors

- Review
- problems
- composite capacitor →
- synthesis

Progress Through Quality Education

24