

Unit - II

2.7 Thevenin's and Norton's Theorem

Dr.Santhosh.T.K.

Progress Through Quality Education

Syllabus

UNIT – II

14 Periods


DC Circuit Analysis: Voltage source and current sources, ideal and practical, Kirchhoff's laws and applications to network solutions using mesh analysis, - Simplifications of networks using series- parallel, Star/Delta transformation, DC circuits-Current-voltage relations of electric network by mathematical equations to analyse the network (Superposition theorem, Thevenin's theorem, Maximum Power Transfer theorem), Transient analysis of R-L, R-C and R-L-C Circuits.

AC Steady-state Analysis: AC waveform definitions - Form factor - Peak factor - study of R-L - R-C -RLC series circuit - R-L-C parallel circuit - phasor representation in polar and rectangular form - concept of impedance - admittance - active - reactive - apparent and complex power - power factor, Resonance in R-L-C circuits - 3 phase balanced AC Circuits

Progress Through Quality Education

$$\begin{bmatrix} 19 & + \\ + & 20 \end{bmatrix} \begin{bmatrix} I_a \\ I_b \end{bmatrix} = \begin{bmatrix} 10 \\ 20 \end{bmatrix}$$

Example

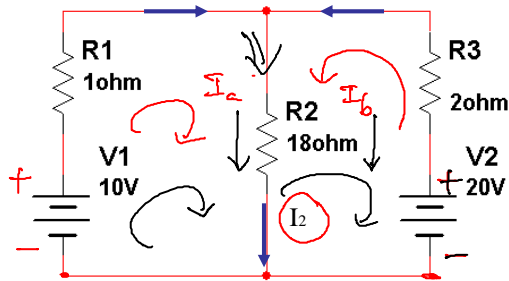

Mesh ②,

$$+10 - 1I_a - 18(I_a + I_b) = 0$$

$$-19I_a - 18I_b = -10$$

Mesh ③

$$20 - 2I_b - 18(I_a + I_b) = 0$$

$$-18I_a - 20I_b = -20$$

$$18I_a + 20I_b = 20 \quad \text{--- (2)}$$

$$19I_a + 18I_b = 10 \quad \text{--- (1)}$$

$$\begin{bmatrix} 18 & 20 \\ 19 & 18 \end{bmatrix}$$

$$I_a = -2.86$$

$$I_b = 3.571$$

$$\Rightarrow \begin{bmatrix} 19 & +18 \\ +18 & 20 \end{bmatrix} \begin{bmatrix} I_a \\ I_b \end{bmatrix} = \begin{bmatrix} 10 \\ 20 \end{bmatrix}$$

$$I_2 = I_a + I_b = 0.71$$

Online Circuit Simulator

<https://www.circuitlab.com/editor/#>


⇒ <https://www.falstad.com/circuit/>

↓
Visualization

$\textcircled{V} \rightarrow \text{sc}$
 $\textcircled{I} \rightarrow \text{oc}$

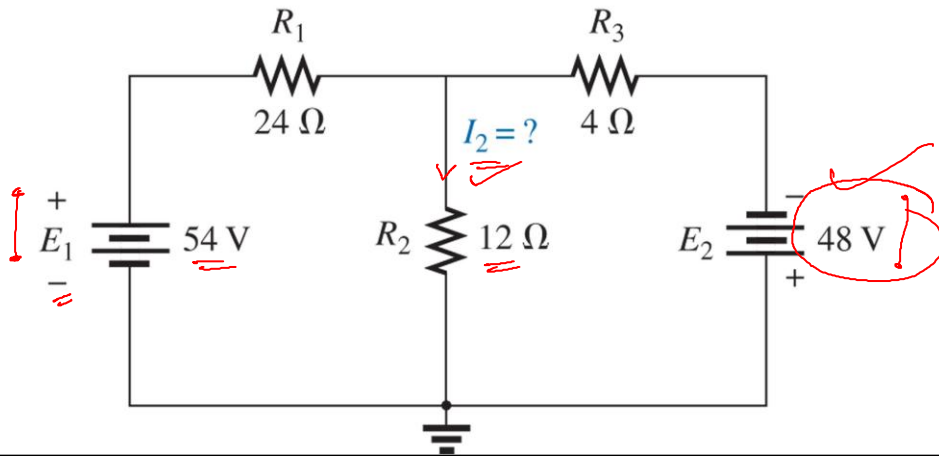Example

- Determine the current in the $12\ \Omega$ resistor using superposition method.




$R_T = R_1 + R_2 \parallel R_3 = 24 + \frac{12 \times 4}{12 + 4} = 24 + 3 = 27\ \Omega$

$I_s = \frac{E_1}{R_T} = \frac{54}{27} = 2\text{A}$

Used current divider rule to determine I'_2

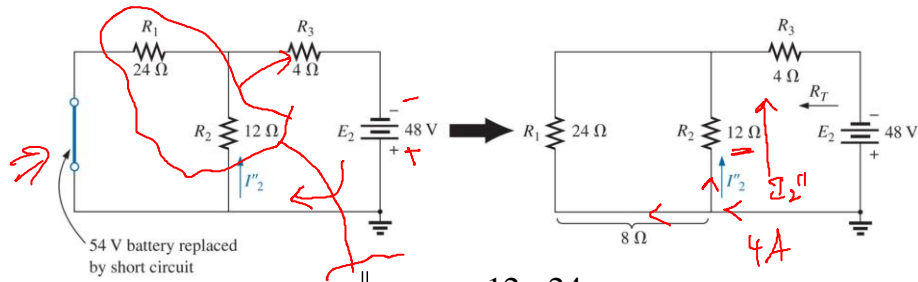$I'_2 = \left(\frac{R_3}{R_3 + R_2} \right) I_s = \frac{4}{4 + 12} \times 2 = 0.5\text{A}$




$$R_T = R_3 + R_2 \parallel R_1 = 4 + \frac{12 \times 24}{12 + 24} = 4 + 8 = 12 \Omega$$

$$I_s = \frac{E_1}{R_T} = \frac{48}{12} = 4 \text{ A}$$

Used current divider rule to determine I''_2

$$I''_2 = \left(\frac{R_1}{R_1 + R_2} \right) I_s = \frac{24}{24 + 12} \times 4 = 2.677 \text{ A}$$

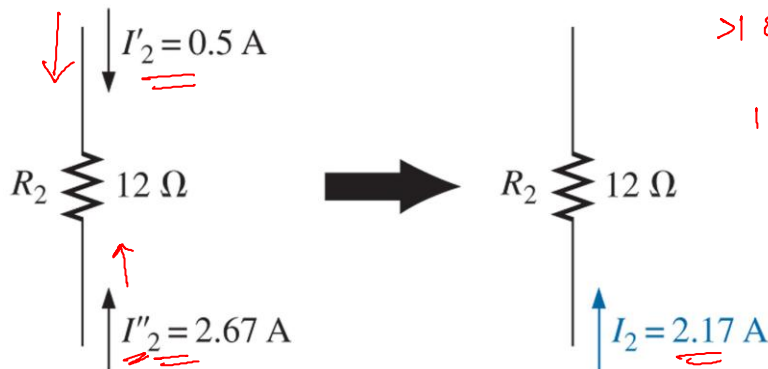To determine current I_2 for the network:



The net current therefore is the difference of the two and in the direction of the larger current:

$$I_2 = I''_2 - I'_2 = 2.667 - 0.5 = 2.167 \text{ A}$$

Superposition

> 1 source

↓
1 source at a time
↳ other sources off

(V) → SC

(I) → OC

↓
Individual response


↓
Algebraic sum

Thevenin's Theorem

Thevenin's Theorem state that,


An active network having two terminals A and B can be replaced by a constant-voltage source having an e.m.f E and internal resistance r . The value of E is equal to the open-circuit potential difference between A and B with the load disconnected and the source of e.m.f replaced by their internal resistance.

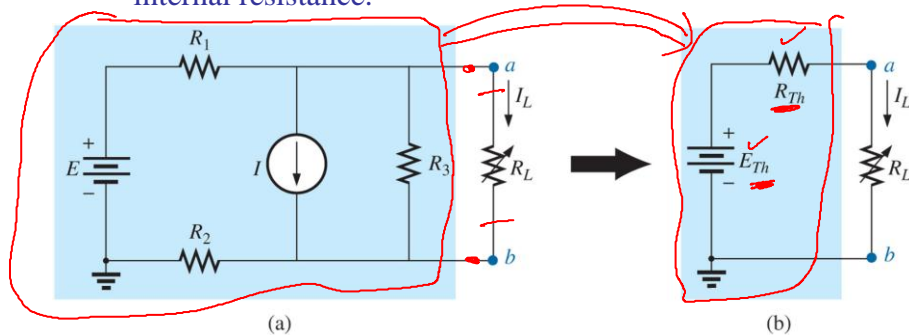$V \rightarrow SC$
 $I \rightarrow \infty$




Thevenin's Theorem Procedure

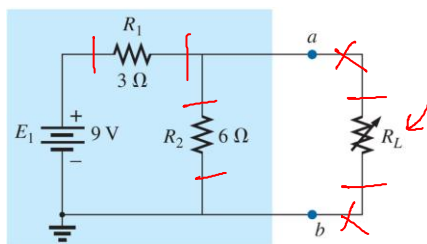$V \rightarrow SC$
 $V = 0$
 $I \rightarrow I_{sc}$
 $I \rightarrow \infty$
 OC



Original

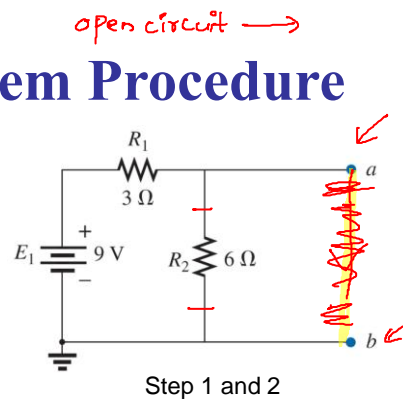

Step 1 and 2

	OC	SC
I	0	I
V	V	0

Step 1: Remove the load resistor R_L .


Step 2 : Mark the terminal as a and b. We have an open circuit across terminal a and b.

E_{Th} / V_{Th}
 \downarrow
 R_{Th}

Thevenin's Theorem Procedure

- Step 3:
 - Replace the voltage source with a short-circuit equivalent.
 - Calculate the R_{TH}
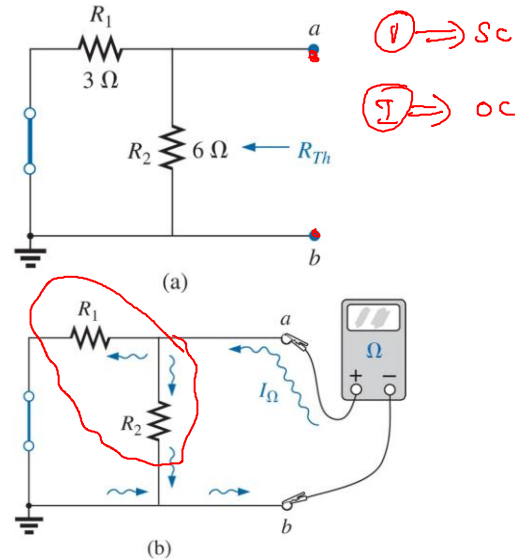
$$R_{TH} = R_1 \parallel R_2 = \frac{3 \times 6}{3 + 6} = \underline{\underline{2\Omega}}$$




- Step 4:
 - Put back the voltage source. Apply voltage divider rule to find V_{TH}

$$E_{Th} = \frac{R_2}{R_2 + R_1} \times E = \frac{6 \times 9}{6 + 3} = \frac{54}{9} = 6V$$


- Or using Mesh current analysis:

<p>Loop 1</p> $\left. \begin{aligned} 9 - 3I - 6I &= 0 \\ 9 - 9I &= 0 \\ 9 &= 9I \\ I &= 1A \end{aligned} \right\}$	<p>Loop2</p> $\left. \begin{aligned} -E_{Th} + 6I &= 0 \\ -E_{Th} + 6(1V) &= 0 \\ E_{Th} &= \underline{\underline{6V}} \end{aligned} \right\}$
---	--

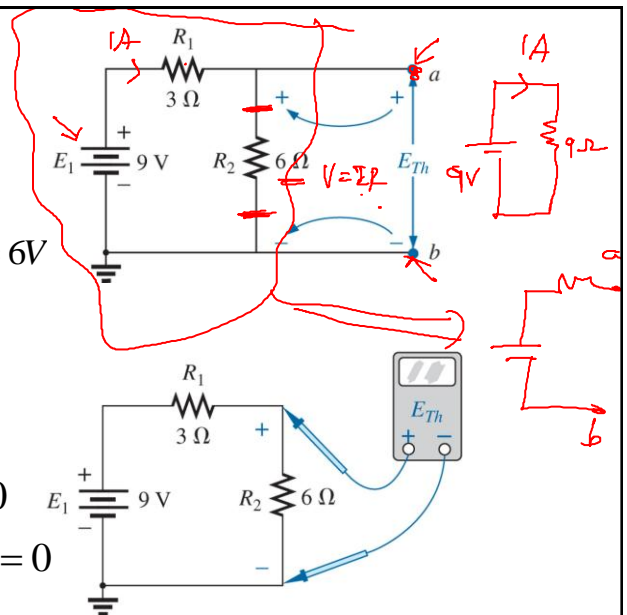

Thevenin's Theorem Procedure

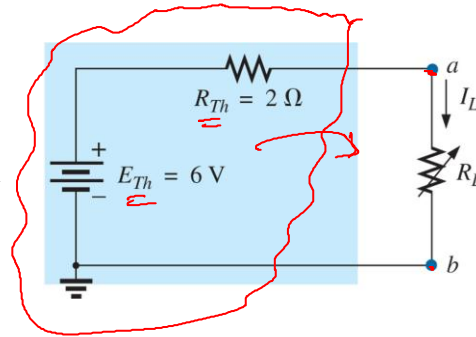
- Step 5:
 - Draw the Thevenin equivalent circuit.
 - Placed the R_L Across terminal a and b.
- Addition:
 - If require to measure current I_L ,



$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

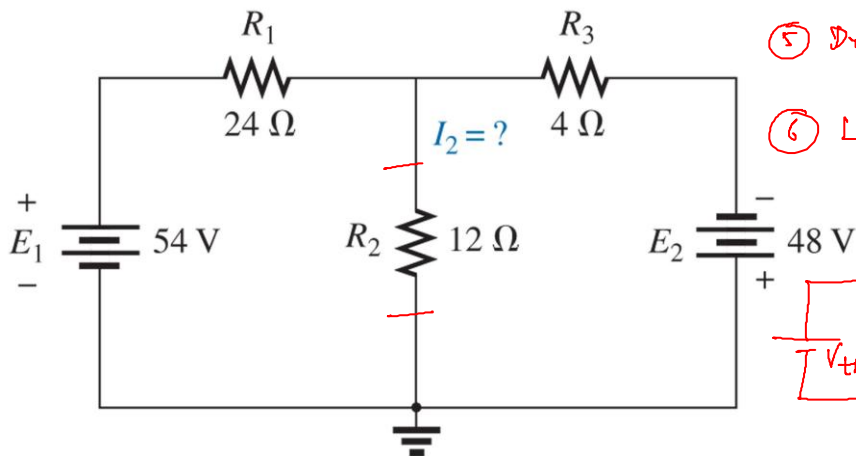Example 4

- Determine the current in the 12 Ω resistor



① Remove R_L

② Turn-off Sources

③ R_{Th}

④ V_{Th}

⑤ Draw Thevenin's equivalent

⑥ Load current



$$R_{TH} = R_1 \parallel R_3 = \frac{24 \times 4}{24 + 4} = 3.42 \Omega$$

Apply KVL to Loop A

$$54 - 24I - 4I + 48 = 0$$

$$102 - 28I = 0$$


$$I = \frac{102}{28} = 3.643A$$

Apply KVL to Loop B


$$54 - 24I + V_{Th} = 0$$

$$V_{Th} = -54 + 24(3.643)$$

$$V_{Th} = 33.432V$$

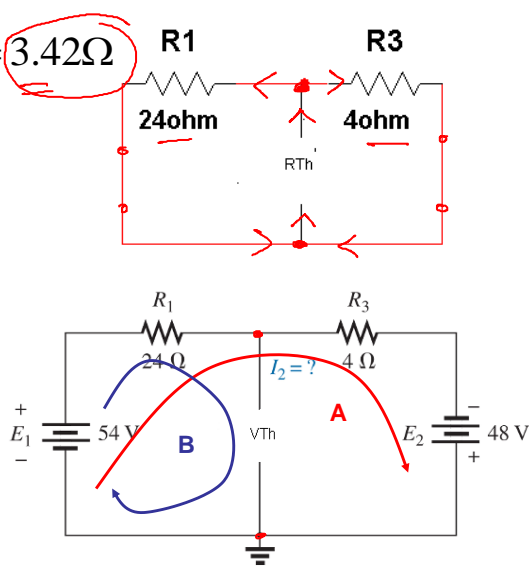


- The Thevenin equivalent circuit

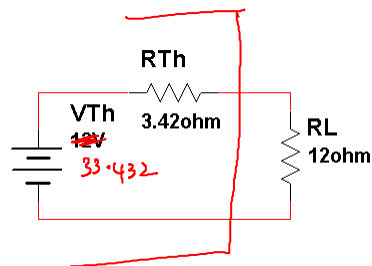

- Current across 12 Ω resistor is:

$$I_{12\Omega} = \frac{33.432V}{3.42 + 12} = 2.168A$$

Practice Problem

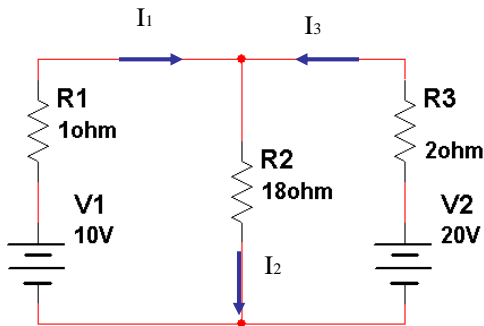

Find the current through 2 ohm resistor using Thevenin's theorem

Summary

Superposition method

↳ Revisited mesh

↳ ⤷ cw current

Thevenin's theorem

$\left. \begin{array}{l} \rightarrow V_{th} \\ \rightarrow R_{th} \end{array} \right\}$

$I_L = ?$

online simulators.